



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 5 Examination in Engineering: January 2024

Module Number: EE5260

Module Name: Hardware Description Language

[Three Hours]

[Answer all questions, each question carries 10 marks]

- Q1 a) What are the key differences between programming languages for Central Processing Units (CPUs) and Hardware Description Languages (HDLs)? [1.0 Mark]
- b) (i). Compare the advantages and disadvantages of Application-Specific Integrated Circuits (ASICs) and Field-Programmable Gate Arrays (FPGAs). [2.0 Marks]
- (ii). Explain the significance of HDL in the Very Large Scale Integration (VLSI) design process. [2.0 Marks]
- c) (i). Name and describe two (02) main components of a VHDL design. [1.0 Mark]
- (ii). Why is drawing a black-box diagram when using VHDL to model digital circuits a good approach? [1.0 Mark]
- (iii). Write the VHDL entity declaration that describes the black-box diagram shown in Figure Q1.c. [3.0 Marks]

 


Figure Q1.c

- Q2 a) Write VHDL models that implement the following Boolean functions using concurrent signal assignments. [3.0 Marks]
- (i). $F(A, B) = \bar{A}B + A + A\bar{B}$
- (ii). $F(A, B, C, D) = (\bar{A} + B) \cdot (\bar{B} + C + \bar{D}) \cdot (\bar{A} + D)$
- b) Write VHDL models that implement the following Boolean functions using conditional signal assignments. [3.0 Marks]
- (i). $F(A, B, C, D) = \bar{A}C\bar{D} + \bar{B}C + BC\bar{D}$
- (ii). $F(A, B, C, D) = (\bar{A} + B) \cdot (\bar{B} + C + \bar{D}) \cdot (\bar{A} + C)$

- c) Provide a VHDL model that can be used to implement the circuit shown in Figure Q2.c.

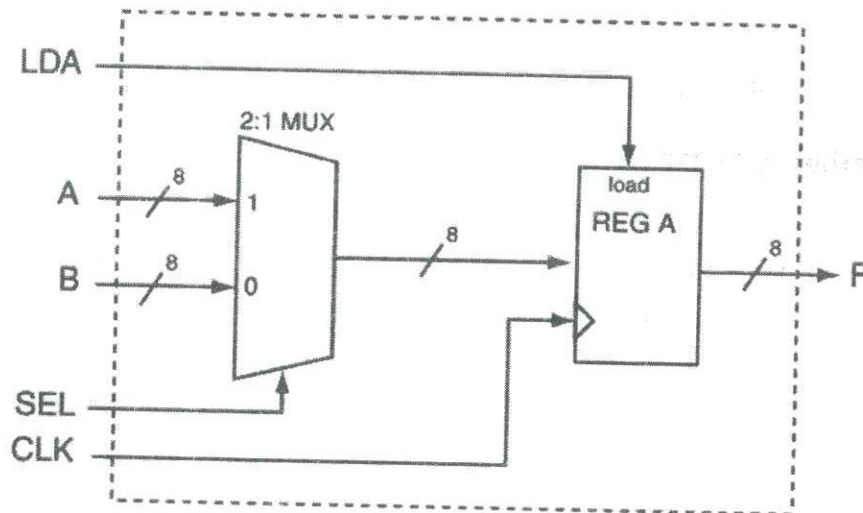


Figure Q2.c

[4.0 Marks]

- Q3 a) Draw the basic flow involved in FPGA design and explain the "Synthesis" step. [4.0 Marks]
- b) Johnson counter, also known as the creeping counter, is an example of a synchronous counter. In the Johnson counter, the complemented (inverted) output of the last flip-flop (FF2) is connected to the input of the first flip-flop (FF0). Figure Q3.a shows a 3-bit Johnson counter. Table Q3.a represents the truth table of the specific counter.
- Copy Table Q3.a. into the answer sheet and fill in all the missing states of FF0, FF1, and FF2. [1.0 Mark]
 - Draw the state diagram of a 3-bit up and down Johnson counter. [2.0 Marks]
 - Write a Verilog module to implement a 3-bit up and down Johnson counter. [3.0 Marks]

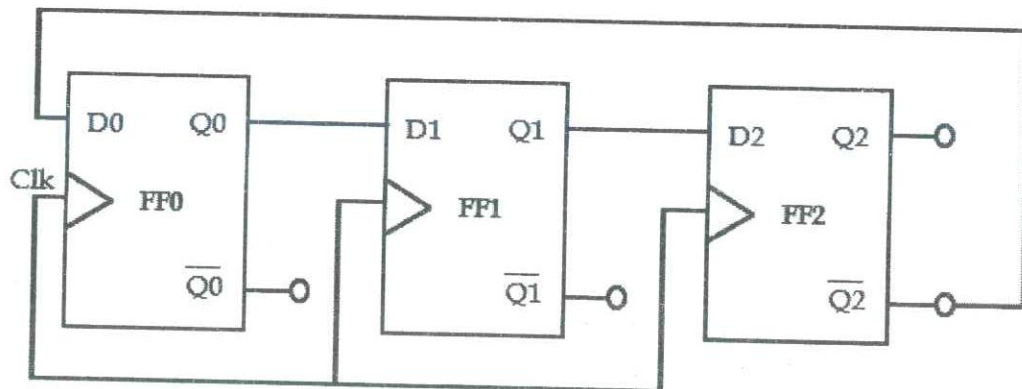


Figure Q3.a: A 3-bit Johnson Counter.

Table Q3.a: The truth table of the 3 – bit Johnson Counter.

Clk	FF0	FF1	FF2
0	0	0	0
1	1	0	0
2	1	1	0
⋮	⋮	⋮	⋮
	0	0	0

- Q4 a) Briefly explain the “Blocking” and “Non-blocking” assignments of Verilog with examples. [2.0 Marks]
- b) Explain the “Incomplete specification” in Verilog designs. [1.0 Mark]
- c) (i). Design an 8-bit ALU in Verilog that supports addition, subtraction, AND, OR, and XOR operations. Provide the Verilog code for the ALU module. [3.0 Marks]
- (ii). Create a test bench to verify the functionality of the ALU designed in Q4.c.i. for different input combinations and operations (a single stimulus for each operation is adequate). [4.0 Marks]
- Q5 a) Explain the differences in the “always” block when included in a combinational design module and in a sequential design module. [2.0 Marks]
- b) (i). Write a Verilog module to implement a 4 to 1 multiplexer. [2.0 Marks]
- (ii). Design a Verilog module for an 8 to 1 multiplexer by using two 4 to 1 multiplexer designed in Q5.b.i and one 2 to 1 multiplexer. (Hint: The inputs should be fed from the 4 to 1 multiplexer and the final output should be obtained through the 2 to 1 multiplexer.) [4.0Marks]
- (iii). Write a test bench to verify the design of the 8 to 1 multiplexer. [2.0 Marks]